

Knowledge Organiser for Science

Class Two

Key vocabulary	
Word	Definition
Electricity	The flow of an electric current through a material, e.g. from a power source through wires to an appliance.
Appliances	A piece of equipment or a device designed to perform a particular job, such as a washing machine or mobile phone.
Battery	A device that stores electrical energy as a chemical. Two or more cells joined together form a battery
Circuit	A pathway that electricity can flow around. It is based around wires and a power supply. Examples of components (parts) you can add in to a circuit are bulbs, switches, buzzers and motors

Appliances


Many everyday **appliances** rely on **electricity** for them to work. Some **appliances** use **mains electricity** (are plugged into a socket) and others have a **battery** to make them work. Examples of **mains-powered appliances** include toasters and televisions. **Battery-powered appliances** can include mobile phones and torches.



Umbrella question



How does electricity make things work?

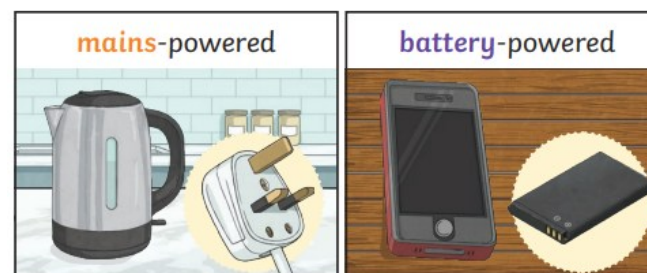

Hinge questions

What is an appliance?

How does a series circuit work?

What makes a circuit complete?

What is an electrical conductor?


What job does a switch do?

Components (Parts) Vocabulary


cell: Normally, we would call this a **battery** but scientifically, this is a cell. Two or more cells joined together form a **battery**.



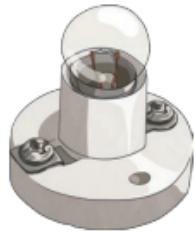bulb: Lights up in a complete **circuit**.



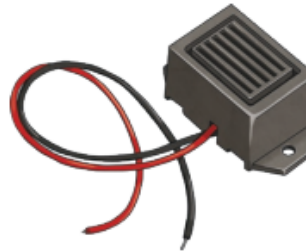
buzzer: Makes a noise in a complete **circuit**.



wires: Used to connect the different components in the **circuit** together.



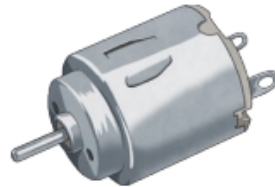motor: Produces movement in a complete **circuit**.




switch: Used to turn other components in the **circuit** on or off.



Materials can be tested in a **circuit** to see if they are **electrical conductors** or **electrical insulators**.



10p = metal = **electrical conductors**

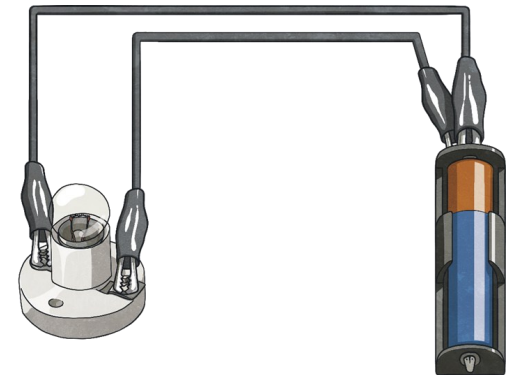


Series **Circuit**

A **circuit** where the components are connected in a loop.

Electricity flows through each component in a single pathway.



Complete **Circuit**

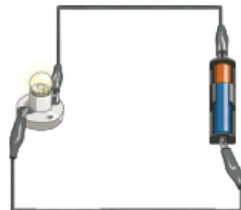

Electricity can flow. The components will work.

Incomplete **Circuit**


There is a break in the **circuit** that prevents the **electricity** from flowing. The components will not work.



Switches can be used to open or close a **circuit**. When off, a switch 'breaks' the **circuit** to stop the flow of **electricity**. When on, a switch 'completes' the **circuit** and allows the **electricity** to flow.



push button switch

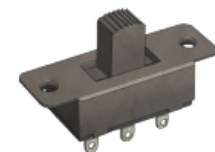

slide switch